


# Charge and Current

$I = Q_v A v$ ,  $Q_v$  is charge density ( $C/m^3$ )  
 $i = \frac{dq}{dt} = \frac{Q}{t}$   
 $q = 1.6 \times 10^{-19}$  (sometimes e)

**Voltage**  
 $V_{high} - V_{low} = \frac{W}{q}$

**Power**  
 $P = \frac{dW}{dt} = \frac{dW}{dq} \cdot \frac{dq}{dt} = Vi$   
 $P = iV = i^2 R = \frac{V^2}{R}$


## Delta Y Transforms

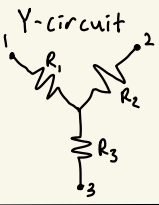

$Y \rightarrow \Delta$ :  $R_A = R_1 R_2 + R_2 R_3 + R_3 R_1$   
 $R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$   
 $R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$

$\Delta \rightarrow Y$ :  $R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$   
 $R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$   
 $R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$

# Current Divider

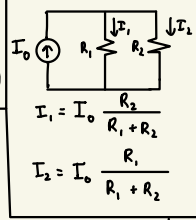

# Concepts

Wheatstone Bridge can be used as a high precision ohmmeter  
 - WB consists of two voltage divider branches in parallel. Output is diff between these branches.  
 - WB cancels common mode voltages, enhancing small voltage changes and making them detectable.


# Waves

$v(t) = A \sin(kx \pm \omega t)$   
 $A =$  amplitude  
 $\lambda =$  wavelength  
 $k =$  wavevector  $= \frac{2\pi}{\lambda}$   
 $T =$  period  
 $\omega =$  angular frequency  $= \frac{2\pi}{T} = 2\pi f$   
 $f =$  frequency  $= \frac{1}{T}$   
 $kx$  and  $\omega t$  are phases and are unitless  
 $v = f\lambda$   
 $f = \frac{v}{\lambda} = \frac{v}{\frac{v}{2f}} = \frac{v}{2L}$


$v = A(\sin(kx)\cos(\omega t) \pm \cos(kx)\sin(\omega t))$   
 when  $x=0, v=0$ . First term becomes zero, second doesn't so  
 $v = A \sin(kx)\cos(\omega t)$   
 when  $x=L, v=0$ , so  
 $\sin(kL) = \sin(n\pi)$ , where  $n$  is any integer  
 $kL = n\pi$   
 $\frac{2\pi}{\lambda} L = n\pi$   
 $\lambda = \frac{2}{n} L$   
 $\frac{\lambda}{2} = \frac{L}{n}$

Standing waves: Two traveling waves in opposite directions  
 $f(0,t) = f(L,t) = 0$ .

# Source Transformation

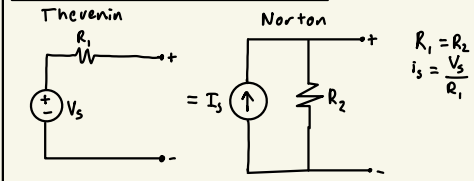

# Wheatstone Bridge Balanced Condition

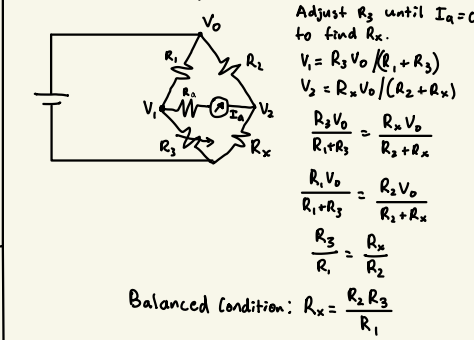

# Mobility & Resistivity

Mobility:  $\mu = \frac{q \tau_{avg}}{m}$  ( $m^2/(V \cdot s)$ )  
 Current Density:  $J = nq\mu E$  ( $A/m^2$ )  
 $n =$  free electron concentration ( $m^{-3}$ )  
 $E =$  electric field (V/m)  
 Conductivity:  $\sigma = nq\mu$  (S/m)  
 Resistivity:  $\rho = \frac{1}{nq\mu}$  ( $\Omega \cdot m$ )  
 $m_e = 9.1 \times 10^{-31}$  kg  $R = \rho \frac{L}{A}$

# Mesh Analysis

$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$

$R_{kk} =$  sum all resistances in mesh k.  
 $R_{jk} =$  negative of sum of shared resistors of meshes j and k.  
 $V_k =$  sum of all voltage sources in k clockwise direction.

# KCL & KVL

**Kirchoff's current law:**  
 The algebraic sum of the currents entering a node must be zero.  
**Kirchoff's voltage law:**  
 The algebraic sum of the voltages around a closed loop must always be zero.

# Nodal Analysis


$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$

$G_{kk} =$  sum of all conductances ( $\frac{1}{R}$ ) connected to node k.  
 $G_{jk} =$  negative of sum of all conductances ( $\frac{1}{R}$ ) between nodes j and k.  
 $I_k =$  sum of current sources entering and leaving node k.


# Equivalent Resistance

Series:  $R_{eq} = R_1 + R_2$   
 Parallel:  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$   
 $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

# Wheatstone Bridge Sensor

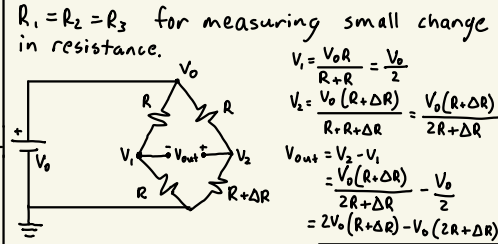

# Superposition

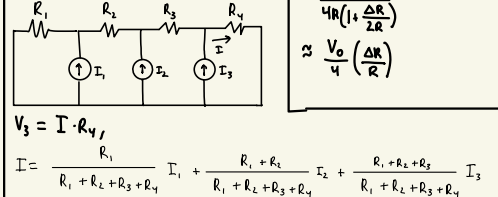

## Capacitors and Capacitance

- Two electrodes separated by an insulator
- Initially, no voltage difference between electrodes
- When connected to a circuit, current flows through the circuit until electrodes have a voltage difference equal to the voltage source (KVL)
- $Q = CV$ , where  $Q$  is accumulated charge and  $C$  is capacitance
- $C = \epsilon A/d$ ,  $\epsilon$  is permittivity of material,  $A$  is area of the plate, and  $d$  is distance between the plates
- Permittivity of Vacuum,  $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$

## Magnitude of Transfer Functions

- Separate into parts, then take square root of all terms squared

## Phase of Transfer Functions


- Separate into parts, then take  $\theta = \tan^{-1}(\frac{\text{Imag}}{\text{Real}})$ , add if multiple parts. Subtract num - denom for each part.

## Inductors

- electrical components that store energy in a magnetic field when current flows
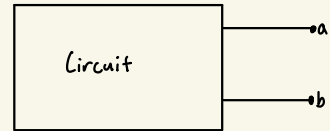
## Thevenin Equivalent

- To find  $V_{Th}$ ,  $a$  and  $b$  should be unconnected. DO KCL!
- To find  $I_{sc}$ ,  $a$  and  $b$  should be connected only with a wire. DO KCL!
- $R_{Th} = \frac{V_{Th}}{I_{sc}}$



## Bode plots

Find magnitude and phase equations then plug in  $\omega = \text{small}$ ,  $\omega = \frac{1}{RC}$ ,  $\omega = \text{large}$  and plot those points

Factor	Bode Magnitude	Bode Phase
Constant $K$	$20 \log K$ 0 dB	$\pm 180^\circ$ if $K < 0$ $0^\circ$ if $K > 0$
Zero @ Origin $(j\omega)^M$	0 dB slope = $20M$ dB/decade	$0^\circ$ $(+90M)^\circ$
Pole @ Origin $(j\omega)^{-M}$	0 dB slope = $-20M$ dB/decade	$0^\circ$ $(-90M)^\circ$
Simple Zero $(1 + j\omega/\omega_c)^M$	0 dB slope = $20M$ dB/decade	$0^\circ$ $(+90M)^\circ$
Simple Pole $(1 + j\omega/\omega_c)^{-M}$	0 dB slope = $-20M$ dB/decade	$0^\circ$ $(-90M)^\circ$

## Equivalent Capacitance

Series:  $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$

Parallel:  $C_{eq} = C_1 + C_2 + C_3$

## Equivalent Inductance

Series:  $L_{eq} = L_1 + L_2 + L_3$

Parallel:  $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$

## Current Flow in a Capacitor

$Q = CV$   
 $i = \frac{dq}{dt} = C \cdot \frac{dV}{dt}$  DO KVL!

$i$  = current flowing through the wires connected to capacitor

$V$  = Voltage across capacitor

## Equivalent Impedance

$Z_R = R$   
 $Z_C = \frac{j\omega C}{1}$   
 $Z_L = j\omega L$

## Power Stored in Capacitors

$P(t) = V \cdot i = V \cdot C \frac{dV}{dt}$   
 $\int_0^{V_s} P(t) dt = \int_0^{V_s} V \cdot C \cdot dV = \frac{1}{2} C V_s^2$

## Time Constant

$\tau = R_{eq} C_{eq}$  or  $\frac{L_{eq}}{R_{eq}}$   
Voltage to dB  
 $dB = 20 \log_{10}(V)$   
 $V = 10^{dB/20}$

## Phasor Notation

Convert everything to cosine

$\sin(x) = \cos(x - 90^\circ)$

For each term:

$8 \cos(6t - 45^\circ) = 8e^{j-45^\circ} = 8\angle -45^\circ$

$8\angle -45^\circ = 8(\cos(-45^\circ) + j\sin(-45^\circ)) = 5.66 - 5.66j$

Magnitude =  $\sqrt{5.66^2 + (-5.66)^2} = 8.00$


Phase Angle:

Draw real vs. imag graph

$\theta = \tan^{-1}(-5.66/5.66) = -45^\circ$

Final phasor:

$8.00\angle -45^\circ = 8e^{j-45^\circ}$

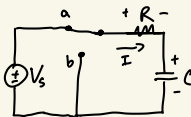

charging @  $t = 0$

$V_s - IR - V_C = 0$

$V_s - RC \frac{dV_C}{dt} - V_C = 0$

$V_s - V_C = RC \frac{dV_C}{dt}$

$\frac{1}{V_s - V_C} dV_C = \frac{1}{RC} dt$

$\int_{V_C(0)}^{V_C(t)} \frac{1}{V_s - V_C} dV_C = \int_0^t \frac{1}{RC} dt$

$-\ln(V_s - V_C(t)) + \ln(V_s - V_C(0)) = \frac{t}{RC}$


$= \ln\left(\frac{V_s - V_C(0)}{V_s - V_C(t)}\right) = \ln\left(\frac{V_s}{V_s - V_C(t)}\right)$

$= \frac{t}{RC}$

$\ln\left(\frac{V_s - V_C(t)}{V_s}\right) = -t/RC$

$1 - V_C(t)/V_s = e^{-t/RC}$

$V_C(t) = V_s(1 - e^{-t/RC})$

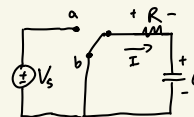

discharging @  $t = t'$

$-V_C - IR = 0$

$-V_C - RC \frac{dV_C}{dt} = 0$

$-V_C = RC \frac{dV_C}{dt}$

$\frac{1}{-V_C} dV_C = \frac{1}{RC} dt$

$\int_{V_C(t')}^{V_C(t)} \frac{1}{-V_C} dV_C = \int_{t'}^t \frac{1}{RC} dt$


$-\ln V_C(t) + \ln V_C(t') = \frac{t - t'}{RC}$

$= \ln\left(\frac{V_C(t')}{V_C(t)}\right) = \frac{t - t'}{RC}$

$\frac{V_C(t')}{V_C(t)} = e^{(t-t')/RC}$


$V_C(t) = V_C(t') e^{-(t-t')/RC}$

$V_C(t) = V_C(t') e^{-(t-t')/RC}$

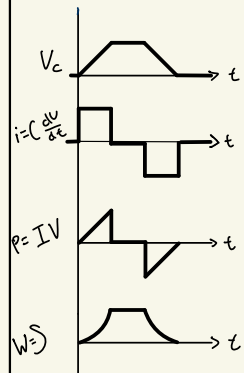

$V_C = L \frac{dI}{dt}$   
 $\int_0^{V_s} \frac{1}{L} dV_C = \int_0^{I(0)} i dt$   
 $\frac{1}{L} \int_0^{V_s} V_C dt = i(0) - i(\infty)$   
 $i(t) = i(0) + \frac{1}{L} \int_0^t V_C dt$   
 $L = \mu N^2 S$   
 $\mu = \frac{\mu_0}{\chi}$   
 $N = \# \text{ coils}$   
 $S = \text{cross-sectional area}$   
 $\mu_0 = 4\pi \cdot 10^{-7} \text{ H/m}$

# Ideal Op Amp Conditions

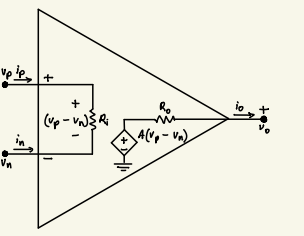

$v_o = A(v_p - v_n)$  b/c  $R_o = 0$   
 $(v_p - v_n) = \frac{v_o}{A}$   
 if  $A \rightarrow \infty$ ,  $v_p - v_n = 0$   
 ①  $v_p = v_n$   
 $(v_p - v_n) = i_p R_i$   
 if  $R_i \rightarrow \infty$   
 ②  $i_p = 0$

## Negative Feedback

Output terminal is connected to the  $v_n$  terminal

## Initial and Final Conditions for Capacitors and Inductors

① At steady state, all voltages and currents in the circuit reach some fixed value.  
 $\frac{dV}{dt} = 0$ ,  $\frac{di}{dt} = 0$

② The voltage through a capacitor and current through an inductor cannot change instantaneously.  
 - requires infinite  $i_c$  or  $v_L$

	Initial Conditions ( $t = 0^-$ )	Final Conditions ( $t = \infty$ )
Capacitors	$v_c(t=0^-) = v_c(t=0^+)$	$i_c(\infty) = C \frac{dv_c}{dt} = 0$ - open
Inductors	$i_L(t=0^-) = i_L(t=0^+)$	$v_L(\infty) = L \frac{di_L}{dt} = 0$ - short

## Second Order Diff EQs

$\frac{d^2x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = 0$   
 $x(t)$  = quantity of interest  
 $\alpha$  = damping factor  
 $\omega_0$  = undamped natural frequency  
 Characteristic Polynomial:  
 $s^2 + 2\alpha s + \omega_0^2 = 0$   
 Homogeneous solution:  
 $x_h(t) = Ae^{s_1 t} + Be^{s_2 t}$   
 $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

## Cases:

- ① Overdamped:  $\alpha > \omega_0$   
 $x_h(t) = Ae^{s_1 t} + Be^{s_2 t}$
- ② Underdamped:  $\alpha < \omega_0$   
 $x_h(t) = e^{-\alpha t} (C \cos(\omega_d t) + D \sin(\omega_d t))$   
 $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
- ③ Critically damped:  $\alpha = \omega_0$   
 $x_h(t) = Ae^{-\alpha t} + Bte^{-\alpha t}$


$x(t) = x_h(t) + x_p(t)$   
 $x_p(t) = x(t = \infty)$ , analyze the circuit in steady state.  
 Use initial conditions  $x(0)$  and  $x'(0)$  to solve for  $A$  &  $B$  /  $C$  &  $D$

## Current Flow in an Inductor

$v_L = L \frac{di_L}{dt}$  do KCL!

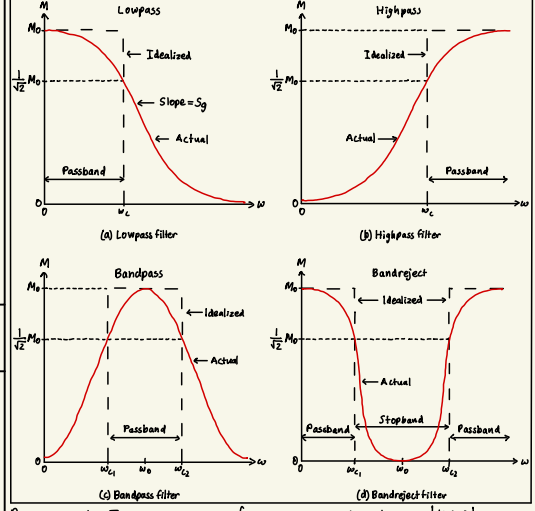
## Filters

- ① Lowpass filters are idealized for low frequencies
- ② Highpass filters are idealized for high frequencies
- ③ Bandpass filters are idealized for a range of frequencies centered at  $\omega_0$ , but cuts off high and low frequencies
- ④ Bandreject filters are idealized for high and low frequencies but not intermediate frequencies.



Resonant Frequency,  $\omega_0$ : frequency at which  $|H(\omega)|$  reaches its maximum  
 Bandwidth,  $B$ : frequency range extending between  $\omega_{c1}$  and  $\omega_{c2}$ , where  $\omega_{c1}$  and  $\omega_{c2}$  are where  $|H(\omega)| = \frac{\max |H(\omega)|}{\sqrt{2}}$  or about -3dB below the max

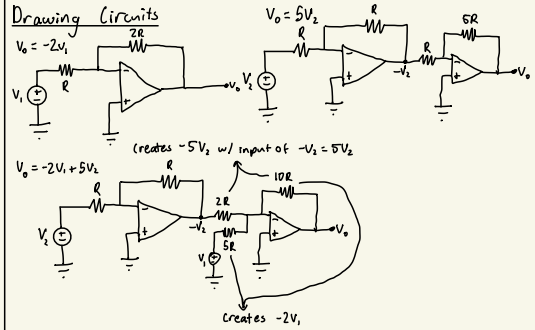Quality factor,  $Q$ : measures how sharp or selective the resonance is.  
 $Q = \frac{\omega_0}{B}$  Higher  $Q$   $\rightarrow$  narrower bandwidth  $\rightarrow$  higher selectivity  
 $Q = \frac{\omega_0 L}{R}$  Lower  $Q$   $\rightarrow$  wider bandwidth  $\rightarrow$  lower selectivity




## RL Circuits

Charging:  $v_L(t) = V_0(1 - e^{-t/\tau})$   
 Discharging: (calculate constant in terms of  $\tau$ , then combine w/ other  $e$  term. Factor exponent to get time shift.
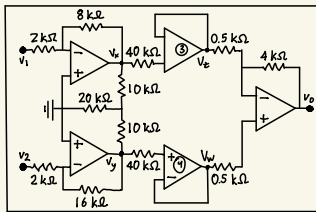
## Steady State

After current has been flowing through a capacitor for a long time, the capacitor will be fully charged and act as an open circuit.  $\rightarrow i_C = 0, v_C = V_0$



After current has been flowing through an inductor for a long time, the inductor will act as a short circuit.  $\rightarrow v_L = 0, i_L = I_0$




$V_A = -\frac{8k\Omega}{2k\Omega} V_1 = -4V$   
 $V_B = -\frac{16k\Omega}{2k\Omega} V_2 = -8V$   
 ③ and ④ are voltage followers since their feedback loop has no resistance.  
 So  $V_3 = V_4 = -4V$   
 $V_5 = V_6 = -8V$

⑤ Negative:  $V_o = -\frac{4k\Omega}{0.5k\Omega} \cdot -4V = 32V$   
 Terminal:  $V_o = \frac{(4 + 0.5)k\Omega}{0.5k\Omega} \cdot -8V = -72V$

$V_o = 32V - 72V$

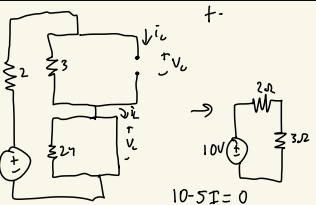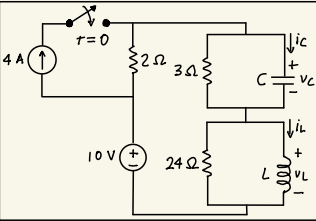

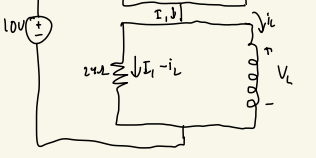$10 - 5I = 0$   
 $I = 2A$   
 $V_c = 2(3) = 6V$



$18 - 2I_1 - V_L = 24(I_1 - I_2) = 0$   
 $18 - 2I_1 - 6 - 24(I_1 - 2) = 0$   
 $I_1 = \frac{30}{13} A$

$\frac{30}{13} = i_C + \frac{V_C}{3}$   
 $i_C = \frac{4}{13} A \rightarrow V_C = 24 \cdot \frac{4}{13} = \frac{96}{13} V$   
 since all current will flow through the capacitor

Design a series RLC bandpass filter with a center frequency  $f_0 = 1 \text{ MHz}$  and a quality factor  $Q = 20$ , given that  $L = 0.1 \text{ mH}$

$$\omega_0 = 2\pi f_0 = 2\pi \times 10^6$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-4}C}} = 2\pi \times 10^6 \rightarrow C = 0.25 \text{ nF}$$

$$20 = \frac{2\pi \times 10^6 \cdot 10^{-4}}{R} \rightarrow R = 31.4 \Omega$$

Determine the 10 dB bandwidth of the filter, which is defined as the bandwidth between frequencies at which the power level is 10 dB below the peak value.

$$M_{BP} [\text{dB}] = -10 \text{ dB}$$

$$20 \log_{10} M_{BP} = -10 \text{ dB}$$

$$M_{BP} = 10^{-0.5} = 0.316$$

$$M_{BP} = \frac{\omega R C}{\sqrt{(1 - \omega^2 L C)^2 + \omega^2 R^2 C^2}}$$

$$\omega_a = 5.87 \times 10^6, \omega_b = 6.81 \times 10^6$$

$$B_{10 \text{ dB}} = 9.4 \times 10^5 \text{ rad/s}$$

$$\text{In Hz: } \omega_a = 5.87 \times 10^6, \omega_b = 6.81 \times 10^6$$

$$\frac{\omega_a}{\omega_0} = 0.93, \frac{\omega_b}{\omega_0} = 1.08$$

$$\omega_a - \omega_b = 2\pi(f_a - f_b)$$

$$\omega_0 = 2\pi f_0 \rightarrow \frac{\omega_a - \omega_b}{\omega_0} = \frac{2\pi(f_a - f_b)}{2\pi f_0}$$

$$\frac{\omega_a - \omega_b}{\omega_0} \cdot f_0 = (f_a - f_b)$$

$$B_{10 \text{ dB}} = 0.15 \text{ MHz}$$

